

Examples of Applications with the Pulse Width Modulator TL5001

Author: Ingrid Kohl

Literature Number: SLVAE05
Date: 02/05/98

IMPORTANT NOTICE

Texas Instruments (TI) reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

TI warrants performance of its semiconductor products and related software to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS.

Inclusion of TI products in such applications is understood to be fully at the risk of the customer. Use of TI products in such applications requires the written approval of an appropriate TI officer. Questions concerning potential risk applications should be directed to TI through a local SC sales office.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards should be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance, customer product design, software performance, or infringement of patents or services described herein. Nor does TI warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used.

Copyright © 1982, 1997, Texas Instruments Incorporated

Contents

1. Introduction	1
2. Step-Down Converters	2
2.1 The inductor as an energy store	3
2.2 The free-wheeling diode.....	4
2.3 The switching transistor	5
2.4 Output capacitance	5
3. The Driver Circuit for the Switching Transistor	6
4. Drain-Source Voltage Limiting	8
5. Pulse Width Modulation	10
6. Circuit Description of the TL5001	10
7. Circuit Design Calculations with the TL5001	12
7.1 Pulse duty ratio	12
7.2 Inductance	13
7.3 Output capacitance	13
7.4 Potential divider at the output	14
7.5 Calculation of the oscillator frequency	14
7.6 Overload protection.....	15
7.7 Dead Time Control (DTC)	15
7.8 Compensating network	17
7.9 Complete circuit diagram.....	21
7.10 List of components.....	23
8. Efficiency	24
8.1 Losses in the switching transistor	24
8.2 Losses in the diode	24
8.3 Losses in the inductor	24
8.4 Overall losses in the circuit.....	24
9. Layout Guidelines.....	25
10. Additional applications Proposals	26
10.1 Step-Up Converter with the TL5001	26
10.2 Step-Down Converter for low output currents	27
11. Summary.....	29
12. References.....	29

List of Figures

Figure 1.1: Block diagram of a Switched Mode Power Supply	1
Figure 2.1: Schematic diagram of a Step-Down Converter	2
Figure 2.2: Inductor current, with continuous and intermittent operation	3
Figure 2.3: Switching behavior of a diode	4
Figure 2.4: Curves of current and voltage in the capacitor	6
Figure 3.1: Driver circuit for MOSFET	7
Figure 3.2: Rise of gate voltage using pull-up resistor or driver circuit	8
Figure 4.1: Limiting the Gate-Source voltage	9
Figure 5.1: Schematic diagram of a pulse width modulator	10
Figure 5.2: Principle of Pulse Width Modulation	10
Figure 6.1: Functional diagram of the TL5001	11
Figure 7.1: Oscillator frequency as a function of resistor R_t	14
Figure 7.2: Dead time control with soft start	16
Figure 7.3: Amplification and frequency characteristics of the output circuit	18
Figure 7.4: Compensating network	19
Figure 7.5: Bode diagram of the compensating network	19
Figure 7.6: Complete circuit diagram of the voltage regulator	22
Figure 9.1: Layout for switching regulators	26
Figure 9.2: Layout proposal for the TL5001	26
Figure 10.1: Step-Up Converter with the TL5001	27
Figure 10.2: Step-Down Converter for low output currents	28

Examples of Applications with the Pulse Width Modulator TL5001

1. Introduction

Switched-mode techniques are used more and more nowadays for the design of power supplies. Switch mode power supplies have considerably higher efficiency when compared to designs employing linear regulators, and can be used for higher output powers. The rectified input voltage in a switching regulator is chopped by means of a switch. The LC network after the switch smoothes this voltage, resulting in a DC voltage at the output. This voltage is controlled by a regulator, such that the end result is a regulated output voltage (see figure 1.1)

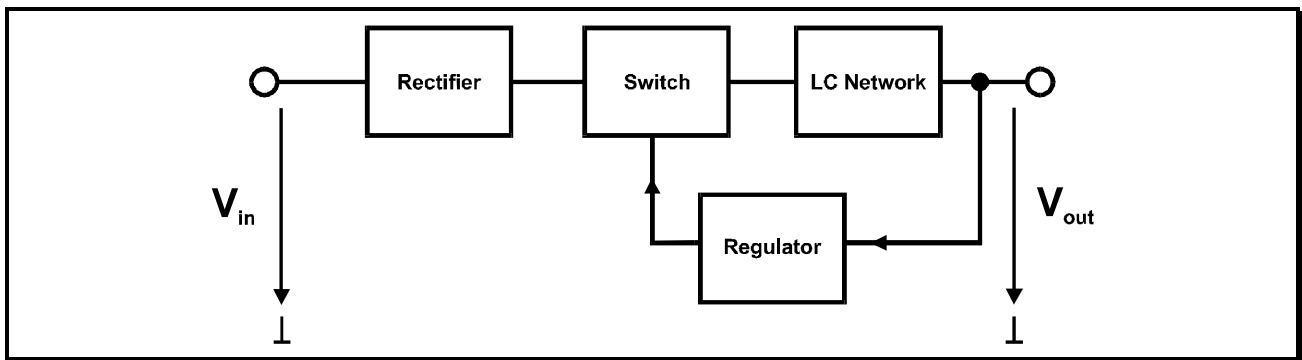


Figure 1.1: Block diagram of a Switched Mode Power Supply

As a result of the high switching frequencies which are involved, very small components can be used. This allows the construction of compact and low-cost power supplies. However, the high frequency switching signals also potentially create interference, and this can only be avoided with careful attention to the design and layout of the circuit.

The configurations of the components which are external to the regulator allow the design of various types of switching regulators. In the following section a step-down converter will be described, in which the output voltage is lower than the input.

2. Step-Down Converters

The circuit diagram of a step-down converter is shown in figure 2.1.

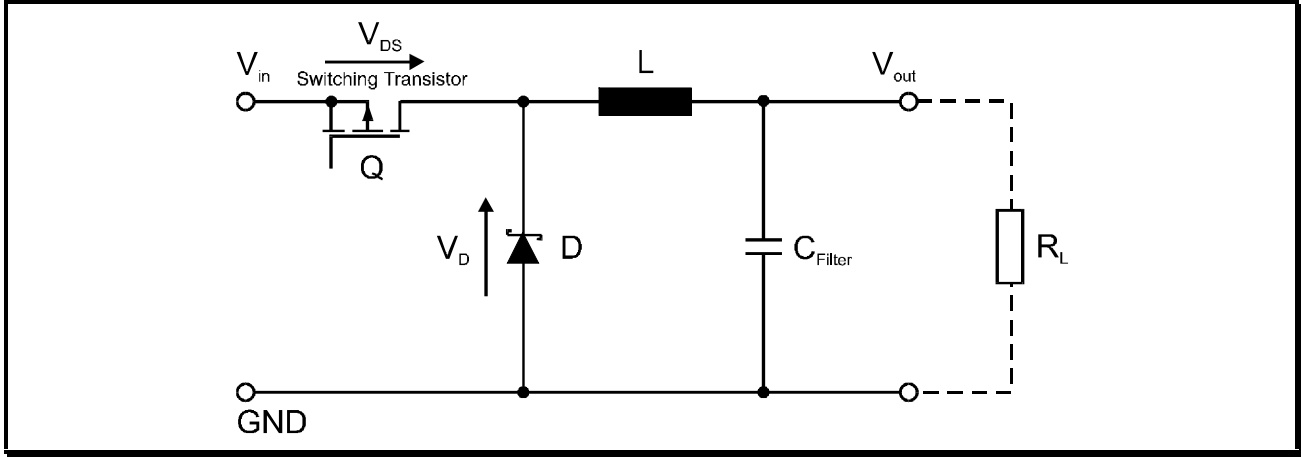


Figure 2.1: Schematic diagram of a Step-Down Converter

The actual voltage converter is made up of a switch (in this case, the transistor Q), the inductor L, the diode D, and the capacitor C. If the switch is closed (transistor Q conducting), current flows via the inductor L to the load. When the switch is open (transistor Q not conducting), the polarity of the voltage across the inductor is reversed, and the current flows via the free-wheeling diode D to the load. The switching transistor is controlled by the output of the regulator.

During the switch-on time t_{on} (transistor Q conducting), the voltage across the inductor can be calculated as follows:

$$V_{in} - V_{DS} - V_{out} = -L \frac{\Delta I}{t_{on}} ; (V_{in} - V_{DS} - V_{out}) t_{on} = -L \cdot \Delta I \quad (1)$$

V_D is the forward voltage of the diode.

V_{DS} is the Drain-Source voltage of the switching transistor, but this will be neglected below.

If the switch is open (transistor Q non conducting), the voltage across the inductor will be:

$$V_{out} + V_D = -L \frac{\Delta I}{t_{off}} ; (V_{out} + V_D) t_{off} = -L \cdot \Delta I \quad (2)$$

The result of equations (1) and (2) is:

$$\frac{V_{out} + V_D}{V_{in} - V_{out}} = \frac{t_{on}}{t_{on} + t_{off}} = \frac{t_{on}}{T} = D \quad (3)$$

This shows that the output voltage V_{out} can be adjusted by means of the pulse duty ratio D.

2.1 The inductor as an energy store

In this circuit the inductor functions as a store of energy. During the time period t_{on} , the current in the inductor rises linearly, up to a value of I_{Lmax} . During the time period t_{off} , the current through the inductor falls again, but retains its direction of flow. A distinction must be made between the two different operating modes: continuous and discontinuous operation (see figure 2.2a and b).

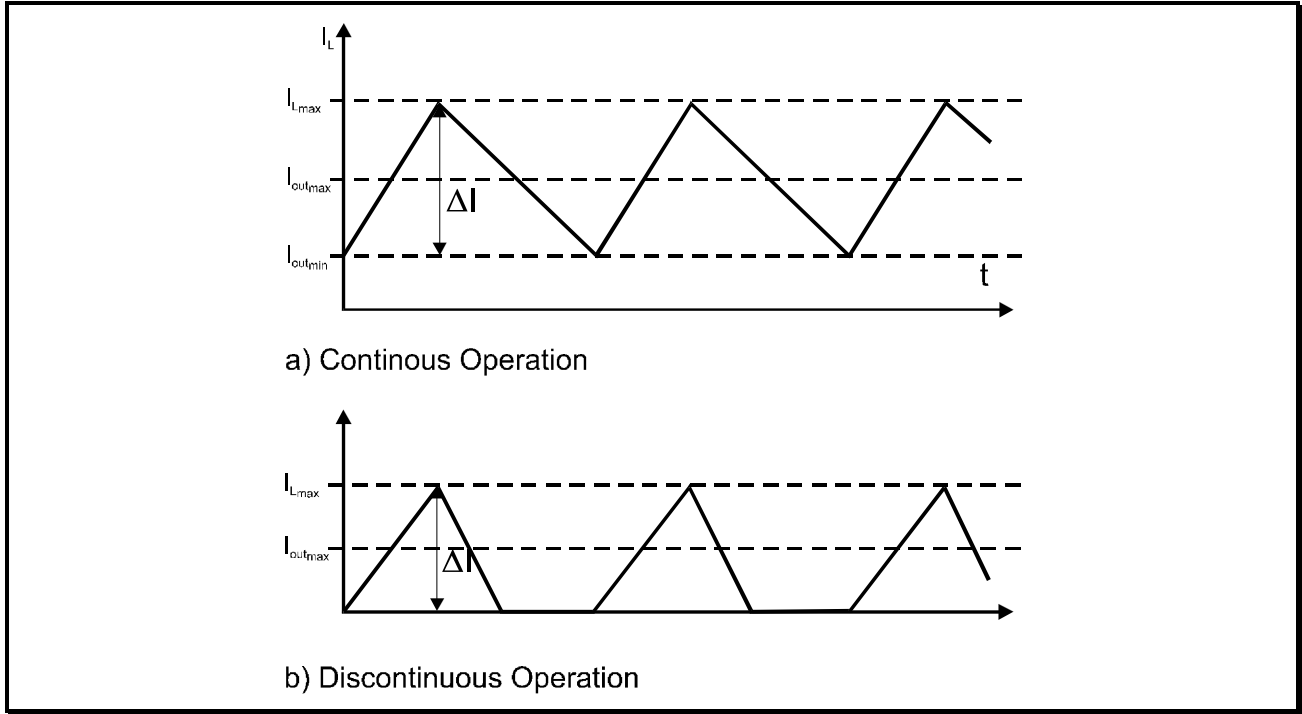


Figure 2.2: Inductor current, with continuous and discontinuous operation

With continuous operation, the current in the inductor does not fall to zero. The change of current in the inductor can be expressed as follows:

$$\Delta I = \frac{1}{L}(V_{in} - V_{out})t_{on} = \frac{1}{L}(V_{out} + V_D)t_{off} \quad (4)$$

The changeover from continuous to discontinuous operation occurs when the curve of the current I_{outmin} in figure 2.2a just touches the zero line. Solving expression (3) for t_{on} and inserting into (4) gives the minimum output current for continuous operation as follows:

$$I_{outmin} = \frac{\Delta I}{2} = \frac{T}{2L} \cdot (V_{in} - V_{out}) \cdot \frac{V_{out} + V_D}{V_{in} + V_D} \quad (5)$$

If the output current sinks further, the flow of current in the inductor will be interrupted. In order to avoid this, the pulse duty ratio must be changed; otherwise the output voltage will rise. Since the pulse duty ratio is limited to a finite switch-on time of the switching transistor, the inductance of the inductor should be chosen to insure that the current in the inductor is not interrupted at the minimum rated current.

The important factors to be considered when designing the inductor are the minimum and maximum load current, the switching frequency, and the voltage drop across the inductor.

$$L = \frac{D}{f \cdot \Delta I} (V_{in} - V_{out}) \quad (6)$$

2.2 The free-wheeling diode

The diode in a switching regulator is used as a free-wheeling diode, maintaining the inductor current, when the switching transistor is turned off. The changeover from the conducting to the blocking state is of great significance with switching regulators, due to the increasing switching losses with increasing frequency. When the transistor is switched on, the diode continues conducting until the reverse recovery time has passed. During this time period, the power dissipation is very high. For this reason fast recovery diodes are needed, which should in particular have a very rapid turn off time.

For applications of this kind, Schottky or epitaxial diodes are appropriate.

Schottky diodes are particularly suitable, because of their low forward voltages and the fast switching times which result from their use of metallic boundaries within the semiconductor. Since they have a low breakdown voltage, Schottky diodes can only be used for low output voltages.

Epitaxial diodes have very fast reverse recovery time, and as a result of their high breakdown voltage can also be used for higher output voltages. Their forward voltage is, however, higher than that of Schottky diodes.

2.2.1 Switching behavior of a diode

 


Figure 2.3: Switching behavior of a diode

When changing over from the conducting into the blocking state, the current in the diode falls with a slope of $-\frac{dI_F}{dt}$. This slope depends on the turn-on speed of the switching transistor. As

soon as the current has reached the maximum reverse current I_{RM} , it rises again at $\frac{dI_R}{dt}$. The current collapses during this period. If the edge is very steep, the collapse of the current takes place very fast, and together with the inductance in the circuit results in high-frequency oscillations. To prevent this from happening, fast soft-recovery diodes can be used which - as a result of their soft switch-off characteristics - avoid the generation of high-frequency interference. Another way of damping these oscillations is to connect a RC network in parallel with the diode.

2.3 The switching transistor

The transistor operates as a switch: either blocking or fully conducting. In this mode of operation, the power dissipation in the transistor is very low, and occurs almost exclusively during the changeover from the conducting into the blocking state. To allow the use of high switching frequencies, in switching regulators a transistor is needed which can be switched on and off very fast.

With bipolar transistors, both types of charge carriers are needed to carry current. During the changeover from the conducting to the blocking state, the charge carriers in the base region must first be removed, resulting in relatively long switch-off times.

In contrast, MOS field-effect transistors use only one type of charge carrier in the conduction of current. Resulting in significantly shorter switching times. The switching time of a MOSFET depends primarily on the Gate-Drain (Miller) capacitance, and which must be charged and discharged during each switching cycle. In order to ensure that this happens very quickly (in a few ns), the gate of the transistor must be controlled by a driver circuit, which provides the current needed to charge and discharge the capacitance, reducing the switching time.

2.4 Output capacitance

The function of the output filter capacitor is to smooth the output voltage, and to stabilize it against sudden changes in the load.

A large capacitance results in a reduction of the ripple at the output.

The value of this capacitance can be calculated from the following expression:

$$C_{\text{Filter}} = \frac{Q}{V_{\text{Ripple}}} \quad (7)$$

The value V_{ripple} is the maximum change of the output voltage, and Q is the charge transferred from the capacitor C_{Filter} to the load during one cycle.

The capacitor will be charged provided that the current in the inductor is larger than the load current I_{out} . The area shaded in figure 2.4 corresponds to the change of the charge Q in the capacitor C_{Filter} .

 


Figure 2.4: Curve of current in the capacitor

$$Q = \Delta I \cdot t = \frac{1}{2} \left(\frac{1}{2} \Delta I \cdot \frac{1}{2f} \right) = \frac{1}{8} \frac{\Delta I}{f} \quad (8)$$

$$C_{\text{Filter}} = \frac{Q}{V_{\text{Ripple}}} = \frac{\Delta I}{8f V_{\text{Ripple}}} \quad (9)$$

The series resistance R_{ESR} and the series inductance R_{ESL} of the filter capacitor should be as small as possible, in order not to increase the ripple on the output voltage. For this reason, a capacitor should be used which has a very low loss resistance, and which also has the necessary high capacitance.

$$R_{\text{ESRmax}} = \frac{V_{\text{Ripple}}}{I_{\text{out}}}$$

As a result of their wound aluminum foil construction, aluminum electrolytic capacitors have a very high series inductance. To reduce this, several capacitors are connected in parallel at the output. As a result of these precautions, the loss resistance R_{ESR} will also be reduced, resulting in a low level of output ripple. The use of tantalum electrolytic capacitors has the additional advantage that they have both a very low series inductance and also a particularly low series resistance.

3. The Driver Circuit for the Switching Transistor

The open-collector output stage of integrated driver circuits for switching regulators used with a pull-up resistor (see figure 3.1a) is not able to deliver the currents needed to charge and discharge the Miller capacitance of the switching transistor. An external driver circuit (see figure 3.1b) should be used. This provides the current needed to charge and discharge the input capacitance of the switching transistor, reducing switching time and increasing efficiency.

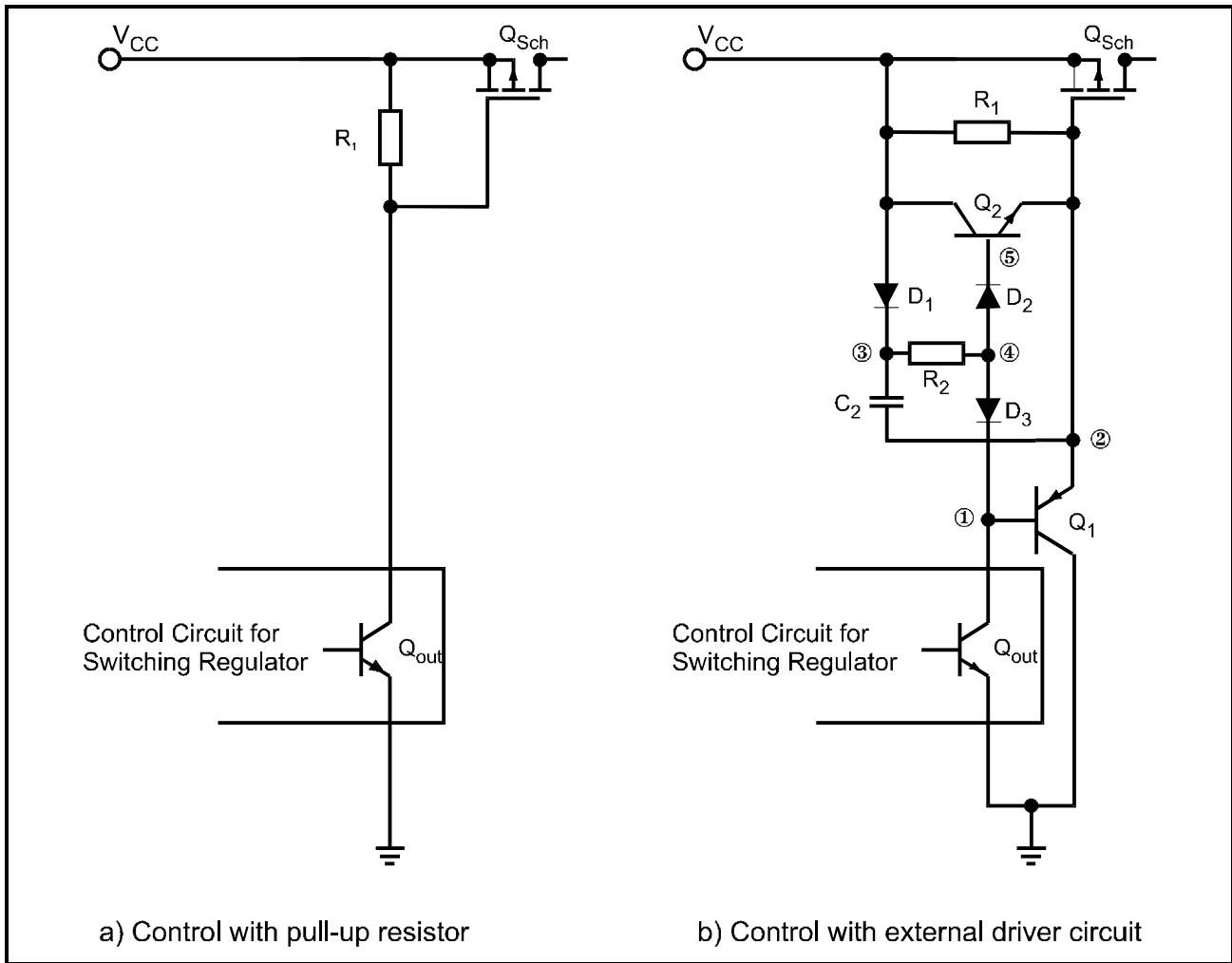


Figure 3.1: Driver circuit for MOSFET

The principle of operation of this circuit can be described as follows.

When the output transistor Q_{out} is in a conducting state, the transistor Q_1 will be driven into conduction, and the Gate-Source voltage of the MOSFET raised correspondingly. The voltage at node 3 will be $V_{C2} = V_{CC} - V_{D1}$, and $V_{BE(Q1)}$ at node 2. In this state, the transistor Q_2 will be non-conducting.

If the output transistor Q_{out} becomes non-conducting, then the transistor Q_1 will also be at a high resistance. The voltage at node 2 increases. Since the voltage across the capacitor can not be changed instantaneously, the voltage at the nodes 2 and 4 will also rise. The transistor Q_2 will conduct. As a result of this kind of feedback (Bootstrap), the transistor Q_2 will be driven very quickly into full conduction.

The difference in the slope of the edges of the rate of rise of the gate voltage V_{GATE} is shown in figure 3.1, with and without a driver circuit.

 


Figure 3.2: Rise of gate voltage using pull-up resistor or driver circuit

The difference is particularly apparent in the rising edge. In the circuit with the pull-up resistor, the rise time depends on the resistor R_1 and the input capacitance of the switching transistor C_{Gate} : $\tau = R_{Pull-up} \cdot C_{Gate}$. When using a driver circuit, the rise time does not depend on the pull-up resistor, but instead on the switching time of the transistors Q_1 and Q_2 . The voltage V_{Gate} at the gate of the switching transistor therefore rises very quickly, and the input capacitance of the MOSFET C_{Gate} is very quickly charged and discharged.

4. Drain-Source Voltage Limiting

With MOS transistors the maximum Gate-Source voltage is usually 20 V. With circuits such as that shown in figure 3.1, the Gate-Source voltage of the switching transistor in the conducting state is about the same as the input voltage V_{CC} . When using an input voltage $V_{CC} > 20$ V an additional circuit must therefore be used to limit the Gate-Source voltage to the maximum permissible value.

The circuit shown in figure 4.1 limits the Gate-Source voltage of the MOSFET to a value which is below the maximum permissible voltage.

The Zener diode Z_1 determines the maximum Gate-Source voltage at the MOSFET. The Zener voltage V_Z of the diode Z_1 is chosen to be high enough to ensure that the MOSFET is driven sufficiently hard to attain the desired on-resistance $R_{DS(on)}$. The transistor J_1 operates as a current source. If the transistor Q_{out} is switched on, and the transistor J_1 thus conducting, then the voltage $V_{CC} - V_{Z1} - V_{D4} + V_{BE(Q2)}$ will appear at node 1. If the transistor is non-conducting, then the voltage at node 1 will again rise to that of the supply voltage V_{CC} .

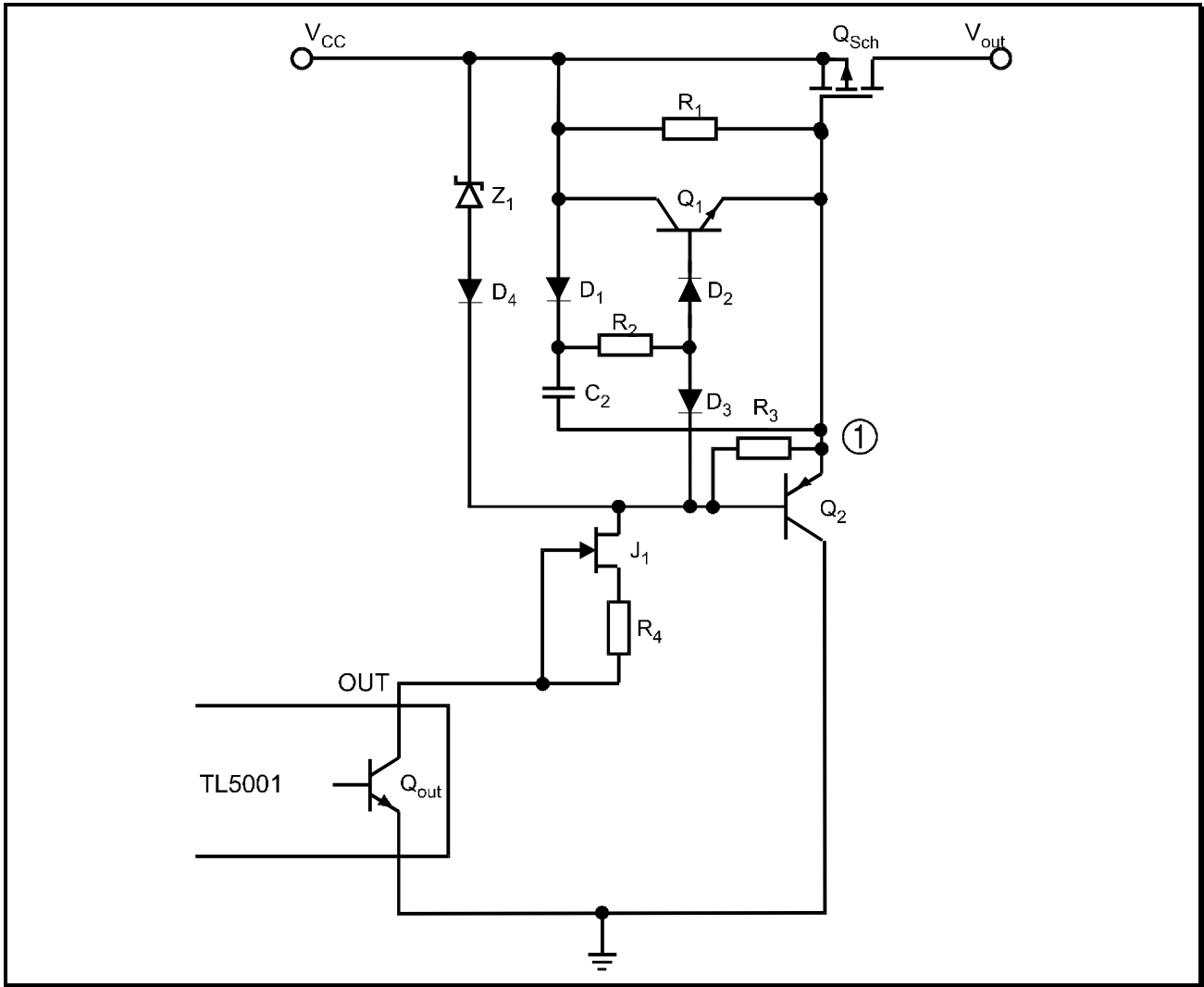


Figure 4.1: Limiting the Gate-Source voltage

5. Pulse Width Modulation

As mentioned above, in a switching regulator the transistor operates as a switch. Pulse width modulation is the method used to control this switching transistor, the on and off time of which is controlled as a function of the output voltage (see figure 5.1).

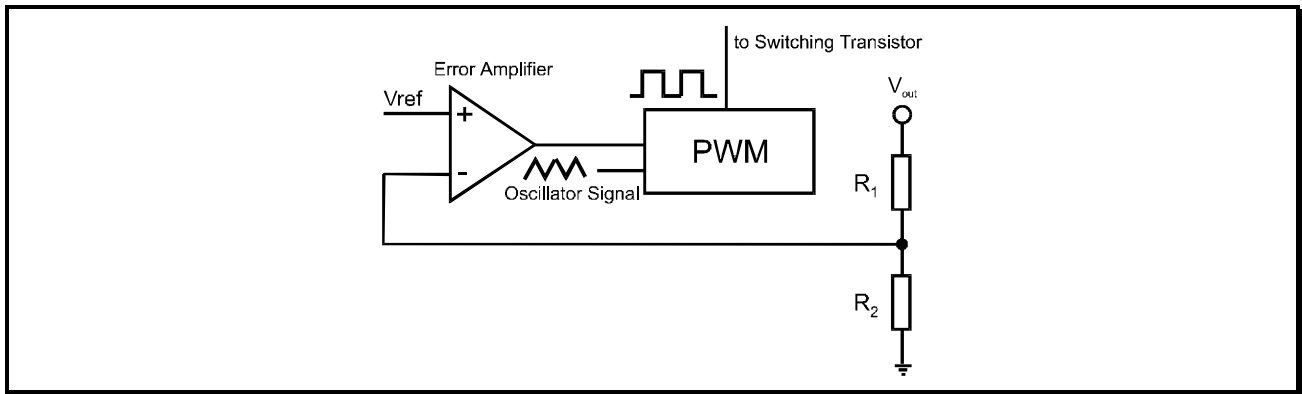


Figure 5.1: Schematic diagram of a pulse width modulator

The output voltage V_{out} which is to be regulated is divided by a resistive divider network R_1/R_2 , and compared with the internal reference voltage in the error amplifier. The difference between the required and the actual value is amplified, and compared in the pulse width modulator with the oscillator signal (see figure 5.1). The output signal of the pulse width modulator is a square-wave pulse, of constant frequency and variable pulse duty ratio. If the amplitude of the output signal of the error amplifier is greater than that of the oscillator signal, then there will be a High signal at the output of the pulse width modulator; if it is less, there will be a Low signal (see figure 5.2).

 


Figure 5.2: Principle of Pulse Width Modulation

6. Circuit Description of the TL5001

The TL5001 includes all of the function necessary in the design of a reliable switching regulator.

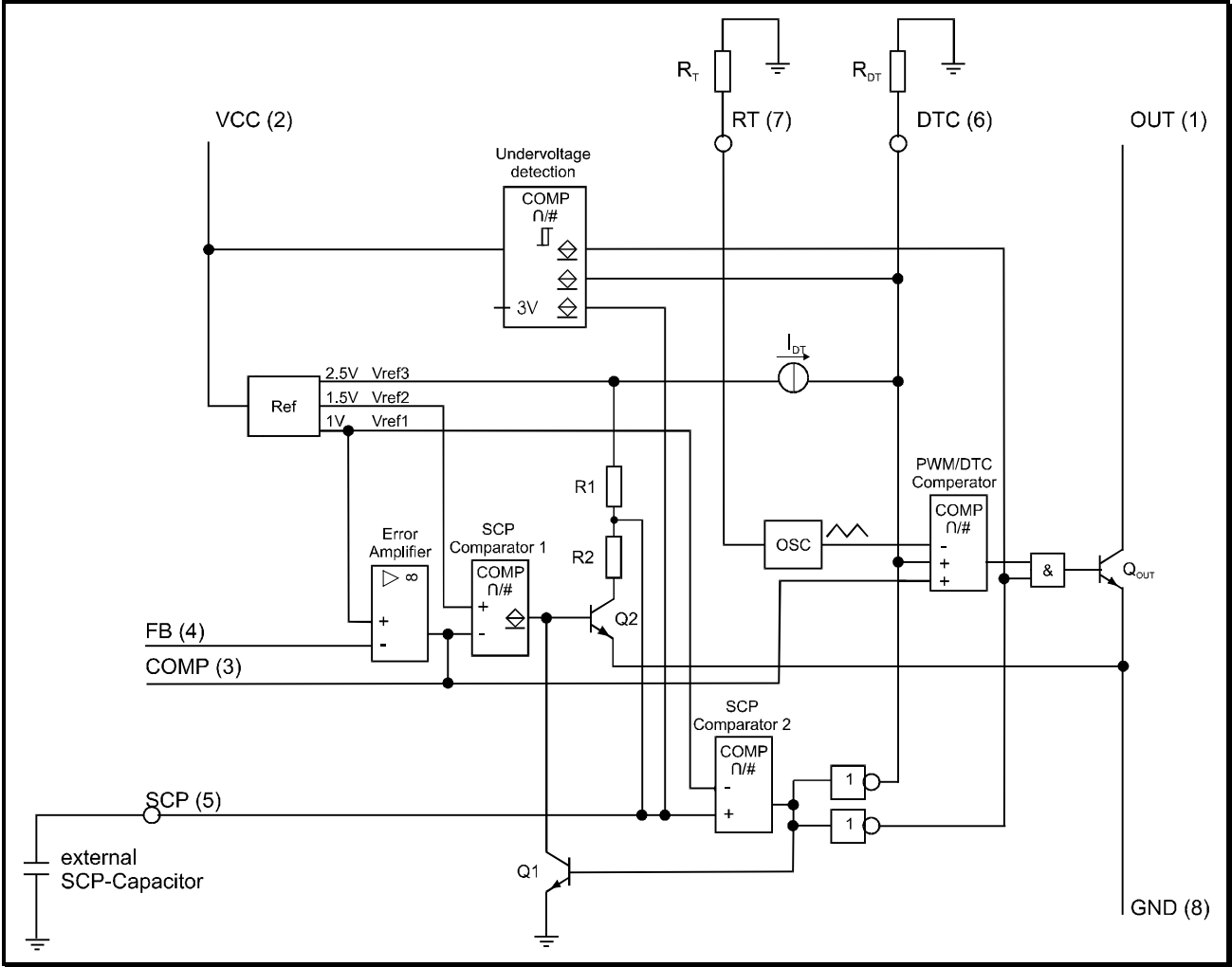


Figure 6.1: *Functional diagram of the TL5001*

The actual value of the output voltage of the switching regulator is fed back to the input FB (Feedback) of the device, and compared with the internally generated reference voltage V_{ref1} in the error amplifier. If the voltage at the input FB (Feedback) is below the reference voltage, then the error amplifier output voltage will be pulled in the direction of the supply voltage of the amplifier; in the opposite case, it will be pulled towards the negative supply voltage (GND). This output signal is now compared in the PWM/DTC comparator with the sawtooth signal of the oscillator OSC and the voltage at the DTC input. If the oscillator signal level is lower than the two other voltages, then the output signal of this comparator will become High; in the opposite case, it will become Low. With a High signal, the output transistor Q_{OUT} will become conducting, and the output OUT will be pulled to ground potential. By means of a constant voltage at the DTC input, which must lie between the minimum and maximum value of the oscillator output voltage, the pulse duty ratio can be limited to a specific value.

If an overload (e.g. a short circuit) occurs at the output of the switching regulator, the output voltage will fall very rapidly, together with the voltage at the input FB. The output signal of the error amplifier will exceed 1.5 V, and generate a Low level at the output of the SCP1

comparator. The transistor Q_1 will become non-conducting and the voltage across the resistive divider network R_1 / R_2 will rise, and charge the external SCP capacitor connected to the SCP terminal. If the voltage across the SCP capacitor rises above 1 V, then the output of the SCP2 comparator will become High, and switch off the output transistor Q_{OUT} via the inverter and the AND gate. The switching regulator will be turned off, and an overload of the circuit avoided. Simultaneously, the transistor Q_1 will be turned on. As a result of the feedback with transistor Q_2 , the short circuit protection will also remain active even when there is no longer a short circuit at the output. The overload protection can only be removed when the supply voltage V_{CC} has fallen to the extent that the under voltage protection has been switched on, or the SCP capacitor has been discharged in another way.

An additional function which has been integrated into the circuit is the undervoltage protection, which is activated at a supply voltage $V_{CC} \leq 3$ V. Below this voltage, reliable operation of the device can no longer be guaranteed. To avoid incorrect operation in this situation, the output transistor is switched off. In the region between the minimum permissible supply voltage of 3.6 V and the operating point of the under voltage protection (≈ 3 V), the regulator will continue to operate, but the regulation characteristics will no longer be defined. In order to avoid a continuous switching on and off of the under voltage protection at low supply voltages, a hysteresis of 200 mV has been built into the device. The danger also exists at too low supply voltages that the operating voltage of the external switching transistor will not be reached. This will then remain non-conducting continuously, and regulation will no longer be possible.

The design of circuits using the TL5001 will be described in more detail in the following section, where the necessary calculations are discussed.

7. Circuit Design Calculations with the TL5001

The design of a regulator circuit with the following characteristics is discussed below.

Input voltage V_{in}	24 - 40 V
Output voltage V_{out}	5 V
Output current I_{out}	5 A
Switching frequency f	200 kHz

The description of the individual components which follows is made assuming the circuit in figure 7.6.

7.1 Pulse duty ratio

The output voltage is derived from the average value of the input voltage, as a result of being switched on and off with a pulse duty ratio of D .

$$V_{out} = D \cdot V_{in} \quad (10)$$

For an input voltage in the range of 24 - 40 V, the pulse duty ratio will be:

$$D_{max} = \frac{V_{out} + V_D}{V_{in \min}} = \frac{5 \text{ V} + 0.7 \text{ V}}{24 \text{ V}} = 24\% \quad ; \quad D_{min} = \frac{V_{out} + V_D}{V_{in \max}} = \frac{5 \text{ V} + 0.7 \text{ V}}{40 \text{ V}} = 14\% ;$$

V_D = Forward voltage of the diode

The switch on-time t_{on} of the switching transistor can be derived from the pulse duty ratio and the chosen switching frequency.

$$t_{on \max} = \frac{D_{\max}}{f} = \frac{0.24}{200 \text{ kHz}} = 1.2 \mu\text{s} ; \quad t_{on \min} = \frac{D_{\min}}{f} = \frac{0.14}{200 \text{ kHz}} = 0.7 \mu\text{s}$$

7.2 Inductance

The inductance must be chosen to be sufficiently large to ensure that the regulator operates continuously over the required range of load current. The circuit should be designed such that continuous operation down to 10% of the maximum output current $I_{out\max}$ is assured.

The minimum alternating current ΔI_{\min} in the inductor (see figure 2.4) will therefore be as follows:

$$\Delta I_{\min} = 2 \cdot 0.1 \cdot I_{out\max} = 1 \text{ A}$$

For the pulse duty ratio, the larger of the values calculated above should be used. This then results in the following value for the inductance:

$$L = \frac{(V_{in} - V_{out}) D_{\max}}{\Delta I_{\min} \cdot f} = \frac{(24 \text{ V} - 5 \text{ V}) \cdot 0.24}{1 \text{ A} \cdot 200 \text{ kHz}} = 22 \mu\text{H} \quad (11)$$

7.3 Output capacitance

The ripple voltage across the output capacitance is determined by the size of the filter capacitor. This ripple voltage superimposed on the output should be < 1 % of the DC output voltage.

The maximum permissible ripple voltage V_{Ripple} at the output is:

$$V_{\text{Ripple}} = V_{out} \cdot 0.01 = 5 \text{ V} \cdot 0.01 = 50 \text{ mV}$$

According to Formula (9), the following value results (assuming ESR=0):

$$C_{out} = \frac{Q}{V_{\text{Ripple}}} = \frac{\Delta I}{8 \cdot f \cdot V_{\text{Ripple}}} = \frac{2 \text{ A}}{8 \cdot 200 \text{ kHz} \cdot 50 \text{ mV}} = 25 \mu\text{F}$$

In addition, account must be taken of the series resistance R_{ESR} of the capacitor. This increases the alternating voltage superimposed on the output. Since the series resistance of an electrolytic capacitor depends on the voltage rating and the capacitance, a capacitor is recommended having a voltage rating which is double the required output voltage, and a capacitance which is about ten times the calculated value.

In this case, a capacitor with a capacitance of 220 μF has been chosen.

7.4 Potential divider at the output

In order to regulate the output voltage, it is first divided down to 1 V with a resistive divider network, and then compared in the error amplifier of the pulse width modulator with the internal reference voltage V_{ref1} .

$$\frac{V_{\text{out}}}{V_{\text{ref1}}} = \frac{R_6 + R_7}{R_7}$$

In this application, the output voltage is 5 V. The maximum resistance is determined by the input current of the error amplifier. With the TL5001, this is 160 nA. If the error resulting from this current should be $\leq 1\%$, then the lateral current in the resistive divider network must be at least 100 times more than the input current of the error amplifier. In this case, a lateral current of about 0.5 mA has been chosen. The values of the resistors which then result are as follows:

$$R_6 = 7.5 \text{ k}\Omega$$

$$R_7 = 1.87 \text{ k}\Omega$$

The resistors must be of close tolerance (1 %), in order that the required value of the output voltage can be achieved.

7.5 Calculation of the oscillator frequency

The frequency of the oscillator is determined by a resistor R_t at the output RT. The oscillator frequency can be varied over a range of 40 kHz to 400 kHz. The necessary values of resistance can be read from figure 7.1. For a frequency of 200 kHz, a resistance value of $R_t = 47 \text{ k}\Omega$ is chosen.

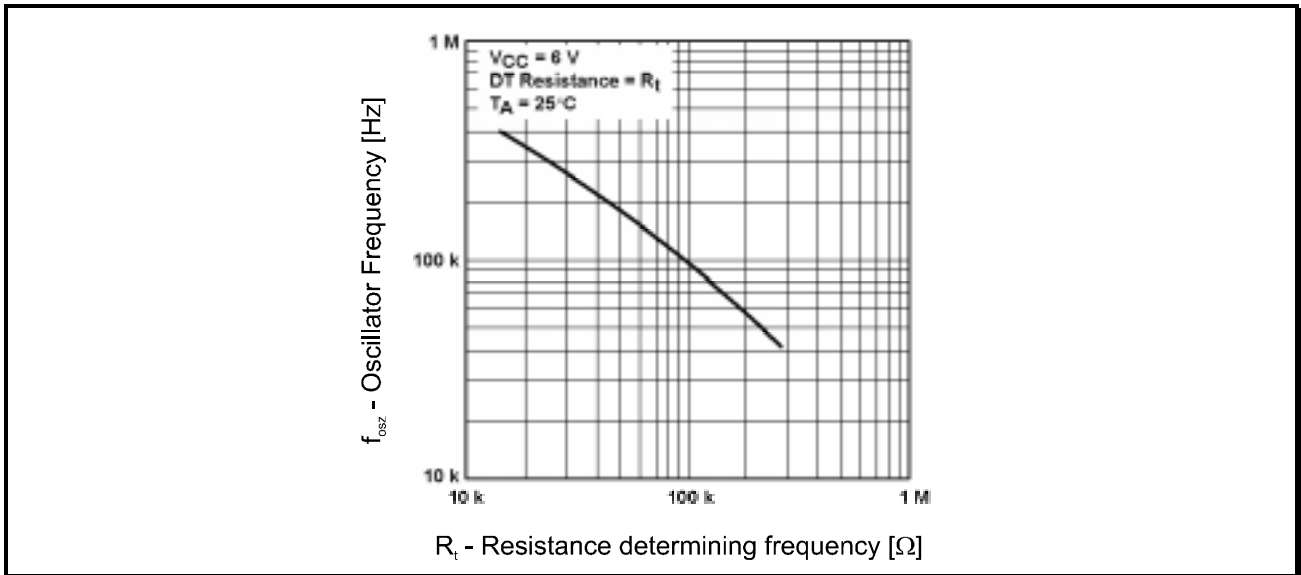


Figure 7.1: Oscillator frequency as a function of resistor R_t

7.6 Overload protection

As mentioned above, the pulse width modulator TL5001 has built-in overload protection, which is activated when there is an overload at the output.

If an overload (e.g. a short circuit) is applied to the output of the switching regulator, the output voltage will collapse. The output signal of the error amplifier (see figure 6.1) will become High. As a result, the output of the SCP comparator 1 will be pulled to Low. The transistor Q_2 will turn off, and the voltage across the resistive divider network R_1/R_2 will rise toward 2.5 V. The capacitor C_{SCP} connected to pin 5 [SCP] will charge up until the voltage at the SCP comparator 2 reaches a value of 1 V. The output of this comparator will become High, and switch off the output via an inverter.

The voltage at the capacitor C_{SCP} rises with an exponential function to:

$$V_{SCP} - 0.185 \text{ V} = V_{ref3} \left(1 - e^{-\frac{t}{\tau}} \right) ; V_{ref3} = 2.5 \text{ V} - 0.185 \text{ V} = 2.32 \text{ V}$$

$$\Rightarrow V_{SCP} - 0.185 \text{ V} = 2.315 \text{ V} \left(1 - e^{-\frac{t}{\tau}} \right) \quad (12)$$

The time constant τ with which the capacitor is charged depends on the capacitor C_{SCP} and the resistor R_{SCP} :

$$\tau = R_{SCP} \cdot C_{SCP}$$

If this formula is inserted in (12) and solved for C_{SCP} , the value of the timing capacitor can be obtained which must be connected to pin 5, as a function of the desired time delay t_{SCP} .

$$C_{SCP} = 12.46 \cdot t_{SCP}$$

When finally determining the time delay t_{SCP} , care must be taken that it is longer than the initiation time of the circuit, otherwise the overload protection will be prematurely activated, and the voltage regulator will not operate.

In this circuit a delay time $t_{SCP} = 50 \text{ ms}$ was chosen, which corresponds to a capacitance of $C = 0.68 \text{ }\mu\text{F}$ in figure 7.6.

7.7 Dead Time Control (DTC)

The pulse duty ratio can be limited by means of the dead time control. This makes it possible to prevent the switching transistor from being switched on during the complete cycle. This is achieved by the use of a resistor connected between Pin 6 and ground. A constant current I_{DT} (figure 6.1) at Pin 6 generates, a voltage drop across the resistor R_{DT} , which compared by the PWM/DTC comparator with the oscillator signal and the voltage at the output of the error amplifier. The use of the dead time control is however not absolutely necessary with a step-down converter, in contrast to step-up converters and flyback regulators.

In this circuit, the maximum pulse duty ratio D is 24 %. For the pulse duty ratio of the dead time control, a sufficiently large value can be chosen, in order to ensure that the performance of the regulator is not adversely affected by limitation of the pulse duty ratio. In this case, the maximum pulse duty ratio is 50%.

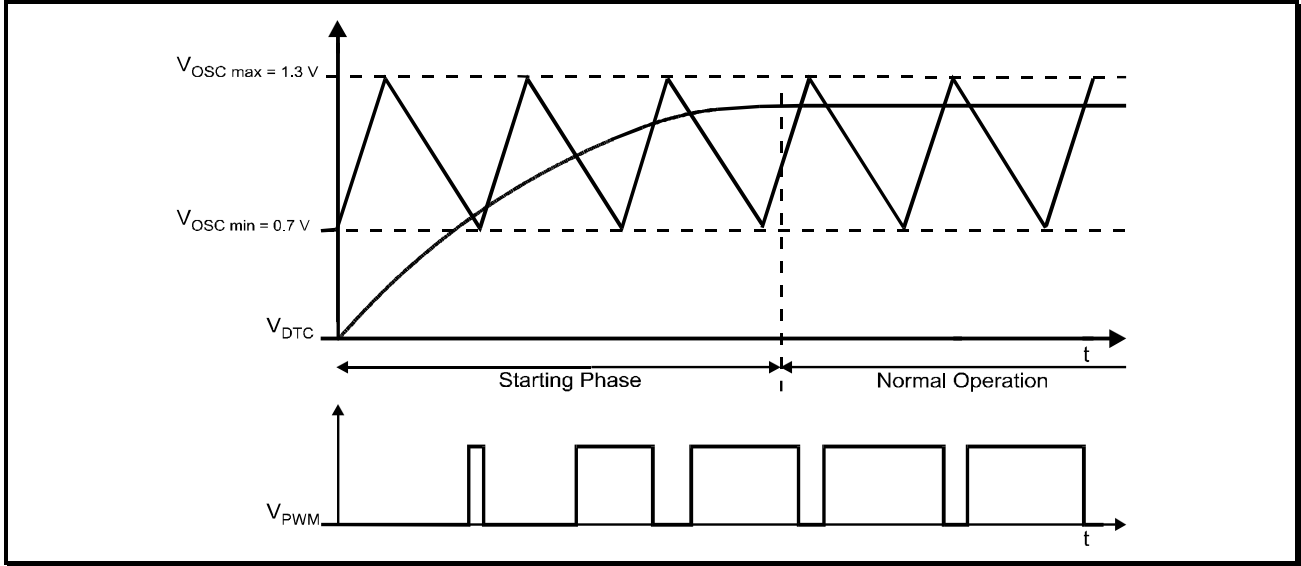


Figure 7.2: Dead time control with soft start

As described in Section 6, the pulse duty ratio is 0 % when the voltage $V_{DT} \leq 0.7 \text{ V}$, and 100 % when the voltage $V_{DT} \geq 1.3 \text{ V}$ or more. The voltage V_{DT} , which must be dropped across resistor R_{DT} in order to achieve a dead time of 50%, can be determined from figure 7.2 (normal operation).

$$V_{DT} = D (V_{OSC_{max}} - V_{OSC_{min}}) + V_{OSC_{min}} = 0.5 \cdot (1.35 \text{ V} - 0.7 \text{ V}) + 0.7 \text{ V} = 1.025 \text{ V}$$

The voltage V_{DT} is generated by the voltage drop caused by the current I_{DT} (figure 5.1) flowing in the external resistor R_{DT} . The same current also flows in the resistor R_t at the oscillator input RT . The external resistance R_{DT} can be calculated with the formula:

$$R_{DT} = (R_t + 1.25 \text{ k}\Omega) \frac{V_{DT}}{1 \text{ V}}$$

In addition to limiting the pulse duty ratio, the DTC input can also be used to implement a soft start of the circuit. At the moment of switching on, the output voltage will not have reached its nominal value. The control amplifier attempts to balance this differential voltage as fast as possible. The result is that the pulse duty ratio immediately reaches its maximum value, leading to a very high current, and therefore a possible overload of the circuit. To prevent this, a capacitor C_{DT} is connected in parallel with the resistor R_{DT} to the input 6 (DTC). As a result, when switching on, the supply voltage V_{DT} increases slowly and the pulse duty ratio rises with a time delay $\tau = R_{DT} \cdot C_{DT}$ (see figure 7.2). In this way, the current when switching on is limited. In order to prevent the overload circuit from operating when switching the regulator on, and the appearance of an apparent overload (output voltage = 0 V), the time constant τ_{DT} should be chosen to be about 10 times larger than the time constant τ_{SCP} .

In this case, a time constant of 5 ms will be assumed. The resulting capacitance is:

$$C_{DT} = \frac{\tau_{DT}}{R_{DT}} = \frac{5 \text{ ms}}{43 \text{ k}\Omega} = 0.1 \mu\text{F}$$

7.8 Compensating network

There is a LC network at the output of the switching regulator, which behaves like a second-order low pass filter. A second-order low pass filter has the property that the phase shift is 180°. If this signal is now applied to the inverting input of the error amplifier, unstable behavior will result. Compensation is added to the error amplifier to delay the phase reversal until the close loop gain is below 0 dB. In order to design the negative feedback loop correctly, the pole points and zero points of the output circuit must first be calculated.

The transfer function of the output circuit at low frequencies is as follows:

$$F(s) = \frac{V_{out}}{V_{in}} = \frac{1}{s^2 LC + 1} \quad (s = 2\pi f)$$

The result of this is a double pole at:

$$f_1 = \frac{1}{2\pi\sqrt{LC_{out}}} = \frac{1}{2\pi \cdot \sqrt{28 \mu\text{H} \cdot 220 \mu\text{F}}} = 2,027 \text{ kHz}$$

At higher frequencies, the influence of the series resistance R_{ESR} of the output capacitor C_{out} becomes apparent. This results in a zero at:

$$f_2 = \frac{1}{2\pi R_{ESR} C_{out}} = \frac{1}{2\pi \cdot 0.035 \Omega \cdot 220 \mu\text{F}} = 20.7 \text{ kHz}$$

The total amplification of this configuration without negative feedback is determined by the maximum change of the output voltage of the circuit, which results from a change of the output voltage of the error amplifier.

The output voltage of the error amplifier will be assumed to be between 0.6 V and 1.4 V, this being slightly above or below the maximum and minimum values of control voltage. The pulse duty ratio of the oscillator is adjusted over a range of 0 and 100 %, by means of an input voltage of 0.7 to 1.3 V. If the minimum voltage of 0.6 V appears at the output of the error amplifier, the pulse duty ratio will be 0 %, and the output voltage of the regulator will fall to 0 V. At the maximum voltage, the pulse duty ratio will be increased to 100 %, and the input voltage will be switched directly to the regulator output. The amplification A can then be calculated as follows:

$$A = \frac{\Delta V_{outmax}}{\Delta V_{Comp}} = \frac{20 \text{ V} - 0 \text{ V}}{1.4 \text{ V} - 0.6 \text{ V}} = 25 \Rightarrow A_{dB} = 20 \cdot \log 25 = 28 \text{ dB} \quad (13)$$

The Bode diagram for the uncompensated control loop is sketched in figure 7.3.

 


Figure 7.3: Amplification and frequency characteristics of the output circuit

The complex pole pair provides a 180° phase shift at f_1 . The zero from the ESR can be seen at the frequency f_2 .

The simplest solution would be to choose the amplification such that the critical frequency is less than 0 dB. This could be implemented with a simple integrator having a reduction of amplification of 20dB / decade. The disadvantage of this method is that, at a low degree of amplification, the output transient response is very poor. For this reason, the frequency at which the amplification is unity should be as high as possible.

A better solution is to arrange the negative feedback as shown in figure 7.4. This compensation network has 3 pole points and two zero points, which can be fixed by means of the correct calculation of the values for the individual components.

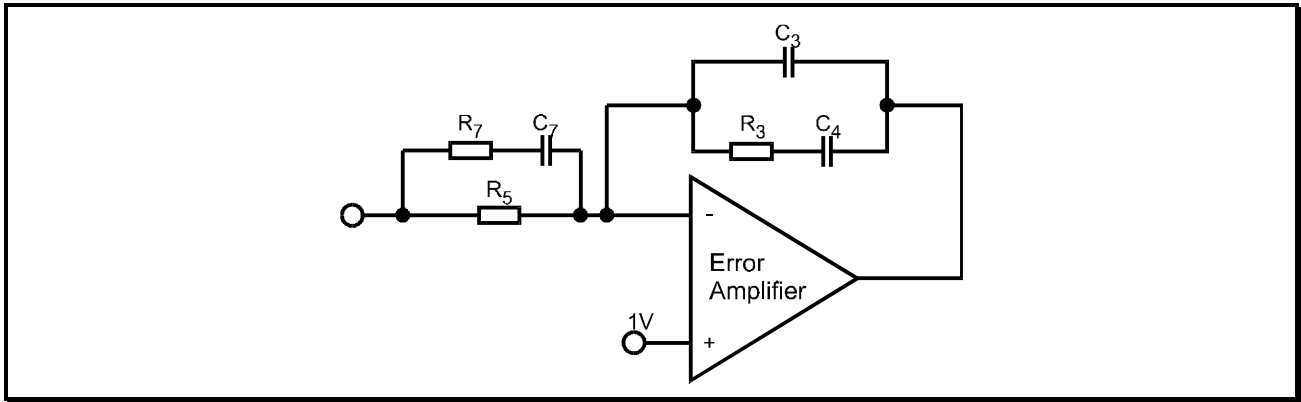


Figure 7.4: Compensating network

The Bode diagram for this compensation network is shown in figure 7.5.

 


Figure 7.5: Bode diagram of the compensating network

The behavior of this feedback arrangement can be described as follows.

The first pole of the feedback is at a frequency of 0. The transfer function is determined by the resistor R_5 and the capacitor C_4 ; C_3 can be neglected, since $C_4 \gg C_3$.

$$\frac{1}{s \cdot R_5 \cdot C_4} = 0$$

The reduction of the amplification of an integrator is 20 dB/decade, and the phase shift is -90° .

In order to compensate the phase shift of 180° due to the pole of the LC network, the compensating network must have a double zero at this frequency f_1 . This means that the amplification must rise at 20dB/decade from the frequency f_1 . The phase shift in this region is $+90^\circ$, corresponding to the behavior of a differentiator. At the zero points of the transfer function, the behavior of the circuit will change from that of an integrator (-20 dB/decade), to that of a differentiator (+20 dB/decade). This means that the resistance R_3 in the feedback loop will be larger than the impedance of the capacitor C_4 , and the impedance of the capacitor C_7 will be larger than R_6 .

The zero of the transfer function is therefore:

$$s \cdot R_3 \cdot C_4 + 1 = 0 \quad \text{and} \quad s \cdot R_5 \cdot C_7 + 1 = 0$$

The next step is that the zero, which results from the series resistance R_{ESR} of the output capacitor at the frequency f_2 , must be compensated with a pole. From this pole, the amplification falls at a rate of 20dB/decade. There is therefore a constant amplification and a phase shift of 0° in the frequency range of f_2 to f_3 . The pole is then attained when the resistance R_8 becomes larger than the resistance of the capacitor C_7 . The pole then becomes:

$$s \cdot R_7 \cdot C_7 + 1 = 0$$

Finally, a pole is introduced at the frequency f_3 , which lies between the previous pole and the oscillator frequency, in order to reduce the amplification at higher frequencies. The pole point is active when the resistance of the capacitor C_3 exceeds the resistance R_3 . This pole is defined as follows:

$$s \cdot R_3 \cdot C_3 + 1 = 0$$

In order to correctly calculate the values for the resistors and capacitors, it must now be established that the total amplification is 0 dB at a frequency of f_2 .

The amplification of the circuit at the frequency f_2 (20 kHz) without feedback is -12 dB. This requires the amplification of the compensating network to be +12 dB at this frequency. At the frequency f_1 , the amplification will be 20 dB lower than at f_2 (see figure 7.5): in other words, it will be -8 dB. C_4 can be calculated from this as follows.

$$\frac{1}{2\pi \cdot f \cdot R_5 \cdot C_4} = 10^{\left(\frac{-8 \text{ dB}}{20}\right)} = 0.398 \Rightarrow C_4 = \frac{1}{0.398 \cdot 2\pi \cdot 2 \text{ kHz} \cdot 7.5 \text{ k}\Omega} = 27 \text{ nF}$$

In the next step, R_3 can be calculated from the zero at 2 kHz:

$$s \cdot R_3 \cdot C_4 + 1 = 0 \Rightarrow R_3 = \frac{1}{2\pi \cdot f_1 \cdot C_4} = \frac{1}{2\pi \cdot 2 \text{ kHz} \cdot 27 \text{ nF}} = 2.9 \text{ k}\Omega$$

Calculations are now given for the values of all the remaining components in the compensating network.

$$s \cdot R_3 \cdot C_3 + 1 = 0 \Rightarrow C_3 = \frac{1}{2\pi \cdot f_3 \cdot R_3} = \frac{1}{2\pi \cdot 100 \text{ kHz} \cdot 3 \text{ k}\Omega} = 531 \text{ pF}$$

$$s \cdot R_5 \cdot C_7 + 1 = 0 \Rightarrow C_7 = \frac{1}{2\pi \cdot 2 \text{ kHz} \cdot R_5} = \frac{1}{2\pi \cdot 2 \text{ kHz}_1 \cdot 7.5 \text{ k}\Omega} = 10 \text{ nF}$$

$$s \cdot R_7 \cdot C_7 + 1 = 0 \Rightarrow R_7 = \frac{1}{2\pi \cdot 20 \text{ kHz} \cdot C_7} = \frac{1}{2\pi \cdot 20 \text{ kHz}_1 \cdot 10 \text{ nF}} = 795 \Omega$$

Since the values which result above are not available in the commonly used range of component tolerances, the following standard values were used:

$$R_3 = 3 \text{ k}\Omega$$

$$R_7 = 820 \Omega$$

$$C_3 = 470 \text{ pF}$$

$$C_4 = 27 \text{ nF}$$

$$C_7 = 10 \text{ nF}$$

7.9 Complete circuit diagram

The complete circuit diagram which results is shown in figure 7.6.

7.10 List of components

Part Number	Component	Value	Manufacturer
U1	TL5001		Texas Instruments
R ₁	Carbon Film Resistor	10 k Ω	
R ₂	Carbon Film Resistor	2.2 k Ω	
R ₃	Carbon Film Resistor	3 k Ω	
R _{DT}	Carbon Film Resistor	43 k Ω	
R ₄	Carbon Film Resistor	43 k Ω	
R ₅	Carbon Film Resistor	7.5 k Ω (1%)	
R ₆	Carbon Film Resistor	1.87 k Ω (1%)	
R ₇	Carbon Film Resistor	820 Ω	
R ₈	Carbon Film Resistor	100 Ω	
C ₁	Electrolytic Capacitor	100 μ F 63 V	
C ₂	Ceramic capacitor	100 nF 63 V	
C ₃	Ceramic capacitor	470 pF	
C ₄	Ceramic capacitor	27 nF	
C ₅	Tantalum electrolytic capacitor	1 μ F	
C ₆	Ceramic capacitor	220 pF	
C _{DT}	Ceramic capacitor	100 nF	
C ₇	Ceramic capacitor	10 nF	
C ₈	Ceramic capacitor	100 nF	
C _{out}	Tantalum electrolytic capacitor	4 x 47 μ F 10 V	
D ₁ - D ₄	Diode	1N914	
D _Z	Zener Diode	22 V	
Q ₁	NPN Transistor	2N2222	
Q ₂	PNP Transistor	2N2709	
J ₁	JFET	BF245C	
Q _{sch}	P channel MOSFET	BUZ171	Siemens
D _{sch}	Diode	BYP100	Siemens
L	Inductor	35 μ H A6161-X002-80	Vacuumschmelze Hanau

8. Efficiency

The efficiency η is defined as the ratio of the output to the input power. With switching regulators, the efficiency is primarily determined by the characteristics of the external components.

$$\eta = \frac{P_{out}}{P_{in}}$$

8.1 Losses in the switching transistor

The losses in the switching transistor depend partly on the energy dissipated while the transistor is being switched, and partly on the voltage drop between Source and Drain while the transistor is switched on. Since the transistor is either switched off or in a saturated state, the last mentioned part is very small.

The losses which result while the transistor is being switched can be calculated from the current that is consumed during switching, and from both the duration of the switching process and the frequency. The static losses when switched on are determined by the resistance R_{DSon} between Source and Drain. The power dissipation of the transistor is therefore made up of the sum of the switching and the static losses.

$$P_{Tran} = P_{stat} + P_{dyn} = (I_{out})^2 \cdot R_{DSon} \cdot \frac{t_{on}}{t_{on} + t_{off}} + Q_{gate} \cdot V_{GS} \cdot f$$

8.2 Losses in the diode

The voltage drop across the diode in a conducting state is mostly responsible for the losses in the diode. The losses as a result of the diode can be calculated as the product of the forward voltage and the load current taken from the output.

$$P_{Diode} = V_D \cdot I_{out} \cdot \frac{t_{off}}{t_{on} + t_{off}}$$

The switching losses which occur at the change over from a conducting into a non conducting state are so small in comparison with the losses during the conducting phase, that they can be ignored.

8.3 Losses in the inductor

The inductor is an additional factor influencing the efficiency of the switching regulator. The losses in the inductor result from the resistance R_{Cu} of the windings (copper losses).

$$P_{Inductor} = (I_{out})^2 \cdot R_{CU}$$

8.4 Overall losses in the circuit

The overall power dissipation in the circuit is the sum of the losses mentioned above in the individual components.

$$P_{\text{Total}} = P_{\text{Tran}} + P_{\text{Diode}} + P_{\text{Inductor}}$$

The overall efficiency which results is:

$$\eta = \frac{P_0}{P_0 + P_{\text{Total}}}$$

9. Layout Guidelines

The mechanical construction of the circuit is just as important as the calculation of the component values for the switching regulator. When designing the layout of the printed circuit board for the regulator, care must be taken that the high frequency switching signals do not generate interference, either in the circuit or in the environment outside.

The metallization which conducts these high frequency switching signals on the circuit board should be kept as short as possible, such that interference can be neither emitted to the outside world nor coupled into the circuit. This will also reduce the inductance of the connections. As a result of the very short switching times the current is changing very rapidly, such that even low values of inductance in the connections can result in considerable voltage drops.

The ground lines of the power section and of the integrated circuit should be run separately, so that the high currents in the output circuit can not influence the regulating circuitry. Both ground lines must however be connected together at a single point, such that different potentials for the two grounds can not occur.

A capacitor of about 0.1 - 1 μF should be connected between the Source pin of the switching transistor and ground, which is able to carry the necessary current when switching occurs. Also in this case it is important to keep the wiring short, and to site the capacitor as close as possible to the Source pin.

The residual ripple in the output voltage results largely from the high inductance and the serial resistance R_{ESR} of the electrolytic capacitor. An improvement can be obtained here by connecting several smaller capacitances in parallel, as these will reduce both the inductance and the series resistance R_{ESR} . The capacitors are connected in a star configuration to the grounding point and to the output voltage line.

The circuit arrangement described above can be seen in figure 9.1.

 


Figure 9.1: *Layout for switching regulators*

Figure 9.2 shows a proposal for the layout of a printed circuit board.

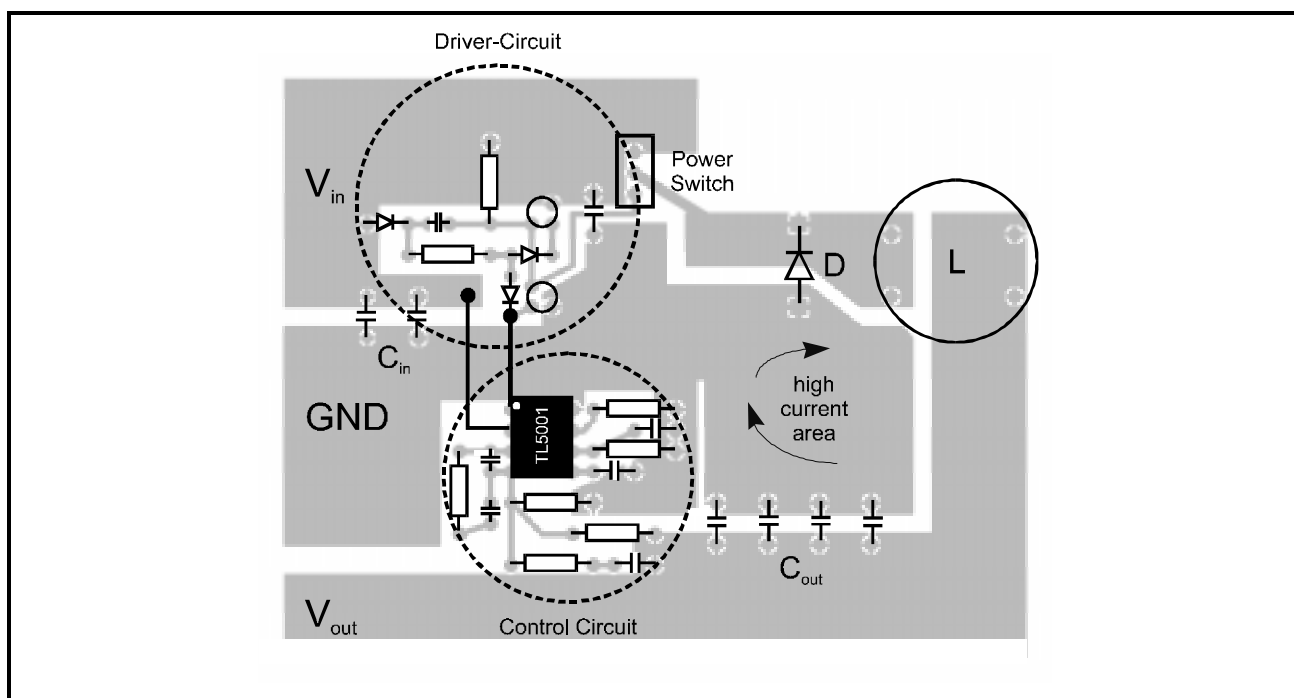


Figure 9.2: *Layout proposal for the TL5001*

10. Additional applications Proposals

10.1 Step-Up Converter with the TL5001

It is also possible to design a step-up converter with the pulse width modulator TL5001. In a step-up converter, energy is stored in the inductor when the switching transistor is conducting. While this is happening, no energy is supplied to the output. In the non-conducting state, the

energy stored in the inductor is passed via the diode to the output circuit. The result is that the output voltage is higher than the input voltage. In order to control the n-channel transistor, the output signal OUT from the integrated circuit must be inverted. In this example a special MOS driver TPS2816 is used, which inverts the signal and also supplies the current needed by the switching transistor in order to switch over.

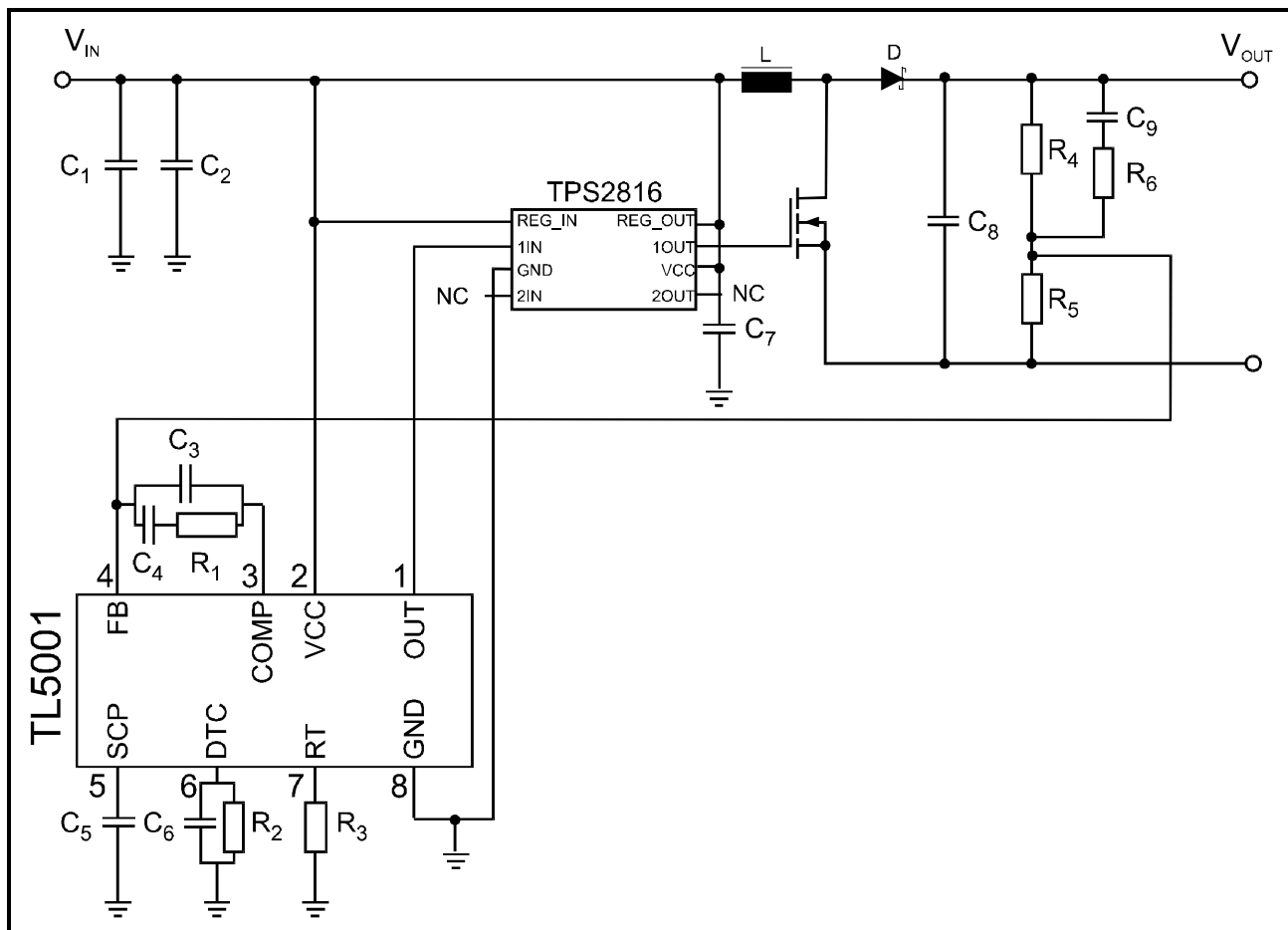


Figure 10.1: Step-Up Converter with the TL5001

10.2 Step-Down Converter for low output currents

If only low currents are needed at the output, then a switching transistor with a very low gate capacitance such as the TPS1101 can be used. In this case no external driver circuit is needed to charge and discharge the gate capacitance. A circuit proposal for a step-down converter of this type can be seen in figure 10.2.

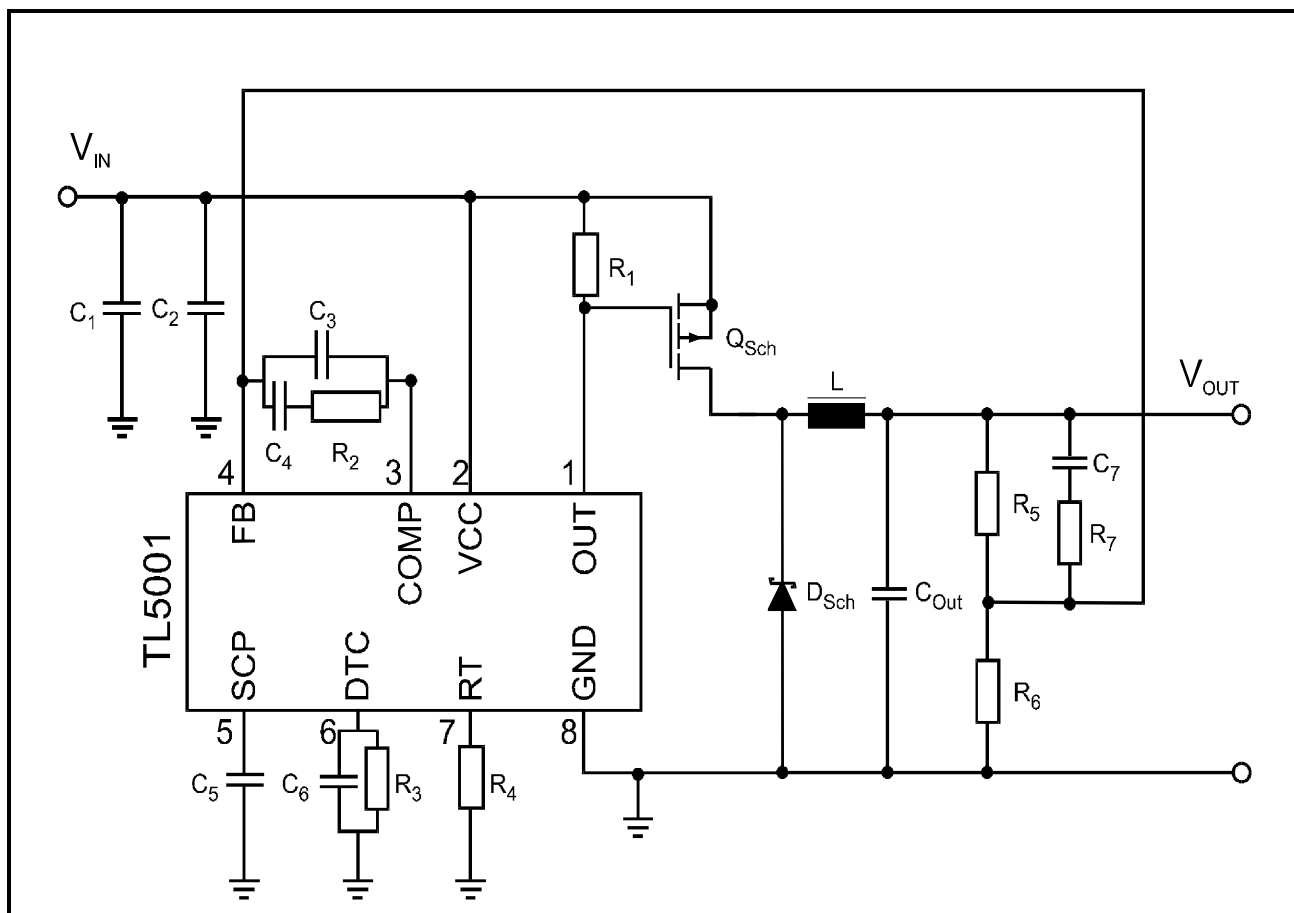


Figure 10.2: Step-Down Converter for low output currents

11. Summary

This Application Report has explained the operation of the pulse width modulator TL5001, and given examples of several applications. This integrated circuit makes it a simple task to design various configurations of switching regulator.

Besides discussing the operation of this pulse width modulator, practical considerations which arise in the development and construction of switching regulators have also been covered.

The three examples of applications:

- a step-down converter,
- an step-up converter,
- and a down converter for low output currents,

demonstrate the use of the TL5001, and include practical proposals for constructing switching regulators.

12. References

Data Sheet TL5001	SLVC084C
Applications report "Designing with the TL5001 PWM Controller"	SLVA034A
Data Sheet TPS28xx	SLVS132C
Power Supply Data Book.....	SLVD002
Internet:	http://www.ti.com